

**Code No: 6CC09**

**Date: 14-Aug-2023 (T.N)**

**B.Tech II-Year I- Semester External Examination, Aug - 2023 (Supplementary)**

**ELEMENTS OF ELECTRONICS ENGINEERING (CSE, IT and BT)**

**Time: 3 Hours**

**Max.Marks:75**

**Note:** a) No additional answer sheets will be provided.  
b) All sub-parts of a question must be answered at one place only, otherwise it will not be valued.  
c) Missing data can be assumed suitably.

**Bloom's Cognitive Levels of Learning (BCLL)**

Remember	L1	Apply	L3	Evaluate	L5
Understand	L2	Analyze	L4	Create	L6

**Part - A**  
**ANSWER ALL QUESTIONS**

**Max.Marks:25**

	BCLL	CO(s)	Marks
1 Derive DC voltage for half wave rectifier.	L4	CO1	[2M]
2 What is the need for biasing a transistor?	L2	CO2	[2M]
3 Define holding current for SCR.	L1	CO3	[2M]
4 Define "bel" and "decibel"?	L1	CO4	[2M]
5 Write the principle in boost type voltage regulator.	L1	CO5	[2M]
6 State the important features of IC 723.	L1	CO6	[3M]
7 Define diffusion current.	L1	CO1	[3M]
8 Why a Field Effect Transistor is called so?	L2	CO4	[3M]
9 What is the use of capacitive coupling.	L2	CO5	[3M]
10 What are the limitations of three terminal regulators?	L2	CO2	[3M]

**Part - B**  
**ANSWER ANY FIVE QUESTIONS. EACH QUESTION CARRIES 10 MARKS.**

**Max.Marks:50**

	BCLL	CO(s)	Marks
11. a) Derive ripple factor and efficiency for Full Wave Rectifier.	L4	CO1	[5M]
b) Write about Breakdown mechanisms in Zener diode.	L1	CO1	[5M]
12. a) Explain the input and output characteristics of Common Emitter configuration with necessary diagram.	L2	CO2	[5M]
b) For a fixed bias configuration given the $V_{cc} = 12V$ , $V_c = 6V$ , $\beta = 80$ , $I_b = 40\mu A$ . Determine $I_c$ , $R_c$ , $R_B$ , and $V_{ce}$ using.	L5	CO2	[5M]
13. a) Explain the V-I characteristics of Silicon Controlled Rectifier.	L2	CO3	[5M]
b) Draw and explain about the Transfer characteristics of n-channel JFET.	L3	CO3	[5M]
14. a) Explain with circuit diagram a negative feedback amplifier and obtain expression for its closed loop gain.	L2	CO4	[5M]
b) Draw and explain the single stage CE amplifier.	L3	CO4	[5M]
15. a) Draw and explain about RC phase shift oscillator.	L3	CO5	[5M]
b) Draw and explain about the Colpitts oscillator.	L3	CO5	[5M]

16.	a) Analyze the block diagram of UPS and discuss its operation.	L4	CO6	[5M]
	b) Design the circuit for voltage doubler.	L6	CO6	[5M]
17.	a) Define PIV for full-wave rectifier.	L1	CO1	[4M]
	b) Explain Current equation for CE transistor configuration.	L2	CO2	[3M]
	c) Define transconductance and amplification factor for JFET.	L1	CO3	[3M]
18.	a) Explain the frequency response of single stage BJT amplifier.	L2	CO4	[4M]
	b) Determine:	L5	CO5	[3M]
	i) The frequency of a Colpitt's Oscillator if $C_1=0.16\mu\text{F}$ , and $L=15\text{mH}$ and			
	ii) If the frequency of oscillation is 10kHz, calculate the value of $C_2$ .			
	c) What is the difference between LMPS and SMPS.	L2	CO6	[3M]

-- 00 -- 00 --