

**Code No:8CC55**

**Date: 17-August-2024 (T.N)**

**B.Tech II-Year II- Semester External Examination, August-2024 (Supplementary)**  
**DIGITAL ELECTRONICS (CSE, IT, CS, AIML, DS and IOT)**

**Time: 3 Hours**

**Max.Marks:70**

**Note:** a) No additional answer sheets will be provided.  
b) All sub-parts of a question must be answered at one place only, otherwise it will not be valued.  
c) Missing data can be assumed suitably.

**Bloom's Cognitive Levels of Learning (BCLL)**

Remember	L1	Apply	L3	Evaluate	L5
Understand	L2	Analyze	L4	Create	L6

**Part - A**  
**ANSWER ALL QUESTIONS**

**Max.Marks:20**

	BCLL	CO(s)	Marks
1 What is the decimal equivalent of hexadecimal number 1A53?	L1	CO1	[2M]
2 Simplify the following Boolean expression: $(A'BC')' + (AB'C)'$	L3	CO2	[2M]
3 Expand POS and SOP	L2	CO3	[2M]
4 Write the characteristic equation for D Flip-flop.	L1	CO4	[2M]
5 What is shift register? Give the classification of them.	L4	CO5	[2M]
6 List out the types of PLD	L6	CO6	[2M]
7 Perform the subtraction operation on 22-7 using 2's complement form..	L3	CO1	[2M]
8 How many states are there in a n-bit ring counter?	L4	CO3	[2M]
9 Compare PROM & PAL.	L2	CO5	[2M]
10 Draw the symbol of universal gates.	L4	CO6	[2M]

**Part – B**  
**ANSWER ANY FIVE QUESTIONS. EACH QUESTION CARRIES 10 MARKS.**

**Max.Marks:50**

	BCLL	CO(s)	Marks
11. a) Convert the following to Decimal and then to Hexadecimal. i. $(1234)_8$ ii. $(11001111)_2$	L1	CO1	[5M]
b) Determine the hamming code 1011011 is received correct it for even parity if any error.	L3	CO1	[5M]
12. a) State and Prove De Morgan's theorem of Boolean Algebra.	L2	CO2	[5M]
b) Simplify the following boolean function using Quine- McClukey method. $F(A,B,C,D) = \sum m(0,1,2,5,7,8,9,10,13,15)$	L3	CO2	[5M]
13. a) Design Full adder using two Half adders.	L5	CO3	[5M]
b) Design a 4 bit binary-to-Gray code converter	L3	CO3	[5M]
14. a) Explain the operation JK master slave flip flop. Explain its truth table	L2	CO4	[5M]
b) Design T flip flop by using SR flip flop.	L3	CO4	[5M]
15. a) Develop 3 bit ripple Asynchronous up counter.	L6	CO5	[5M]
b) Design a 4 bit universal shift register with neat diagram		CO5	[5M]
16. a) Write the differences between PAL and PLA	L1	CO6	[5M]
b) Minimize and implement the Boolean function $F = \sum(0,1,2,3,13,14,15)$ using PROM	L3	CO6	[5M]
17. a) Realize Ex-OR and Ex-NOR gate operations by NOR gates.	L2	CO1	[4M]
b) Express the Boolean function $F = xy + x'z$ in a product of maxterm form	L3	CO2	[3M]
c) Explain the working of a De-multiplexer with the help of an example	L1	CO3	[3M]
18. a) List the difference between latch and flip flop	L3	CO4	[4M]
b) What is the shift register? List out the applications of shift registers	L1	CO5	[3M]
c) Explain short notes about ROM and PROM	L2	CO6	[3M]